

Lecture 18, Feb 28, 2022

Thevenin Equivalent Circuit

- Equivalent circuits allow us to simplify parts of circuits so we still get the same behaviour elsewhere
- Thevenin's Theorem: A linear circuit can be replaced by a series connection of a voltage source (Thevenin voltage) and a resistor (Thevenin resistance) (Thevenin equivalent circuit), to give the same current and voltage outside the circuit
 - This generalizes equivalent resistances and source transformation to an equivalent circuit of any linear element
- The Thevenin voltage is the same as the open circuit voltage between the terminals
 - i.e. remove the load (rest of the circuit) and open the circuit, find the voltage this way and that is the Thevenin voltage
 - The open circuit voltage can be found using any circuit analysis technique (e.g. nodal/mesh analysis)
 - The polarity of the voltage source must match that of the open circuit voltage found
- The Thevenin resistance can be found through 3 different methods:
 1. If the circuit does not include a dependent source (i.e. only resistors and independent sources): deactivate all the *independent* sources (short voltage sources, open current sources); the equivalent resistance is the Thevenin resistance
 2. If the circuit includes at least 1 independent source: find the open circuit voltage V_{oc} and short circuit current i_{sc} ; then $R_{Th} = \frac{V_{oc}}{i_{sc}}$ (V_{oc} and i_{sc} must have directions conforming to PSC)
 - This method is essentially based on source transformation; we find the Thevenin and Norton voltage/current and use source transformation to relate the two by the Thevenin/Norton resistance
 3. Otherwise (applies to any linear circuit):
 1. Deactivate all *independent* sources
 2. Add a test current source of i_T between terminals
 3. Find the voltage across the current source v_T , *not* conforming to PSC
 4. $R_{Th} = \frac{v_T}{i_T}$
- Alternatively, don't deactivate any sources, connect a current source of I_T and find voltage V_T across it; then $V_T = MI_T + N$, and $N = V_{Th}$, $M = R_{Th}$
 - This allows you to find both the Thevenin voltage and resistance by solving just one circuit, but you have to work with I_T as an unknown